# Circuiti Aritmetici 020045 Progetto di un comparatore binario a due bit

Biundo Mattia 19/10/2022


#### 1) Tavola di verità:

A1	A0	B1	<b>B</b> 0	G	E	L
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

•••

### 2) Mappe di Karnaugh:




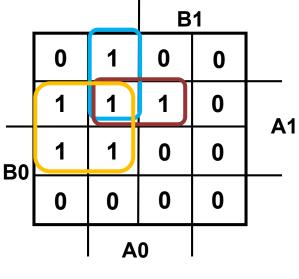


G

G = A1 !B1 + !B0 A0 !B1 + A1 A0 !B0



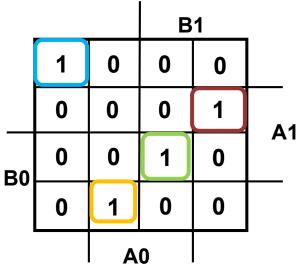

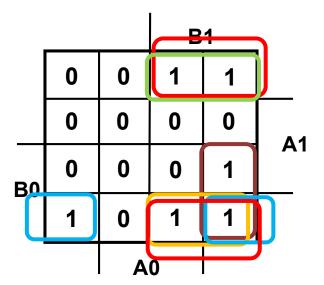E = !B1 !B0 !A1 !A0 + B1 !B0 A1 !A0 + B1 B0 A1 A0 + !B1 B0 !A1 A0




L


L = B1 !A1 + B1 !A0 B0 + !A0 B0 !A1

 $\mathbf{E}$ 

## 3) Schema del circuito:

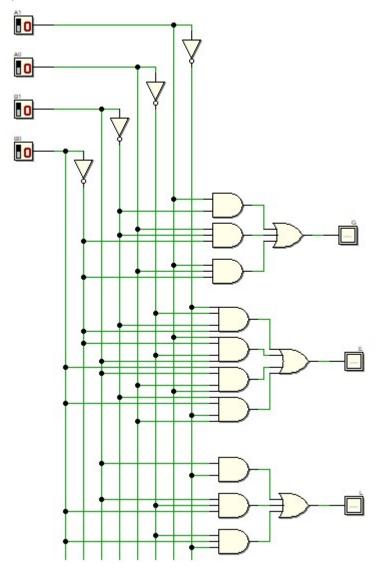

## 4) Diagramma temporale:

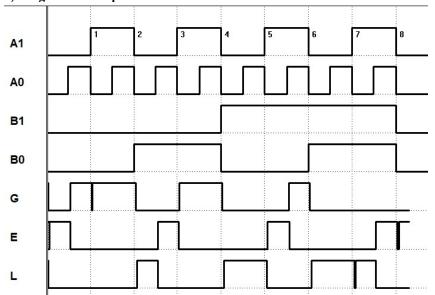

5) Eventuali commenti:	