 


Implementing the Simple MIPS Machine

MIPS has 3 Instruction Types:




The Simple Machine Implements:

R-Types: ADD, SUB, AND, OR, NOR, SLT

I-Types: LW, SW, & BEQ

J-Types: J

Single Cycle Datapath with Control Unit

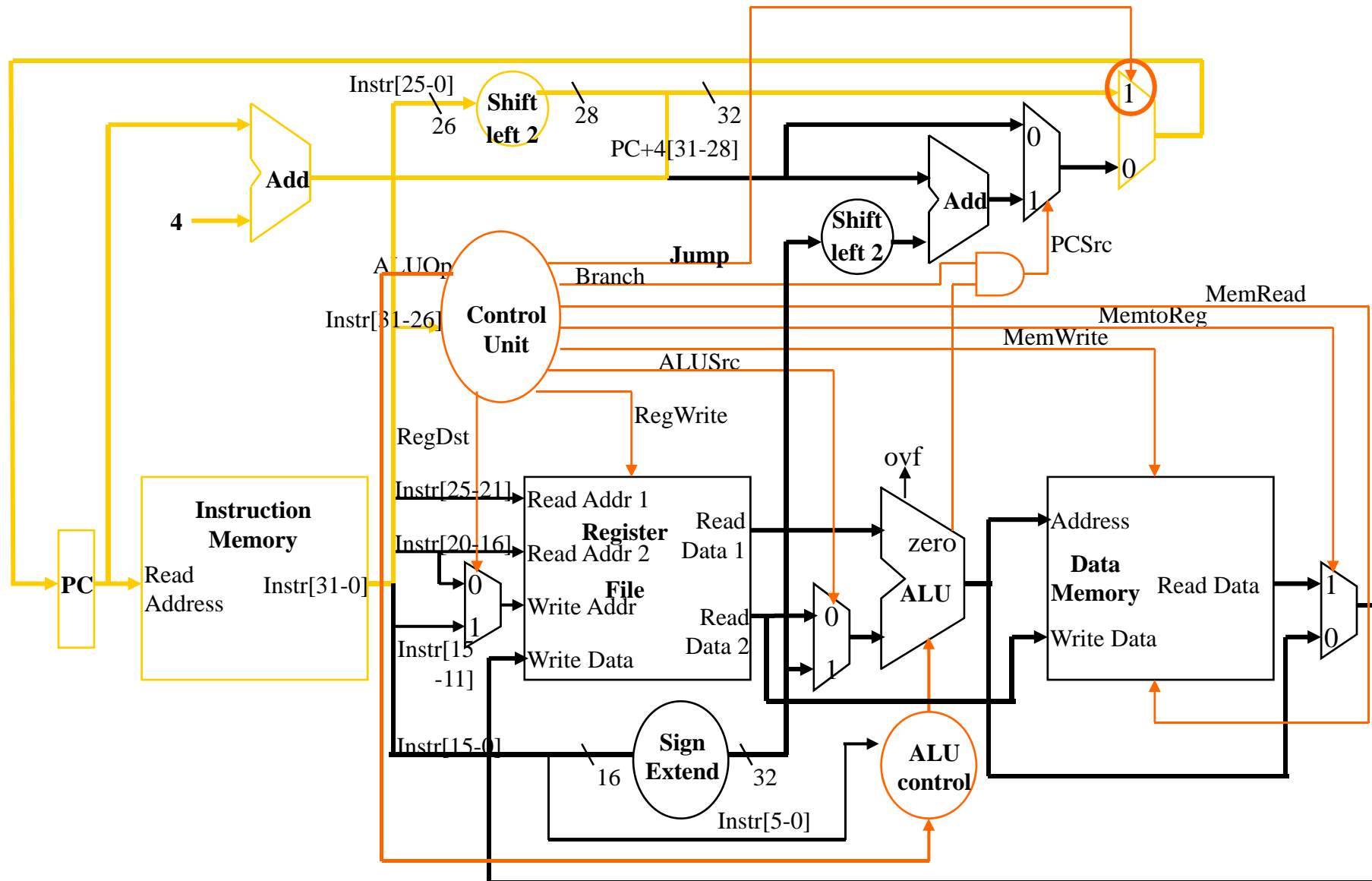

Generating the ALUOp1 & ALUOp0 Signals

ALUOp1 & ALUOp0 are generated from the 6 bit OPCODE:

Instruction Types: Instructions (Opcodes) → ALUOp1 & ALUOp0

R-Type: ADD, SUB, AND, OR, NOR, SLT (000000) → 10

I-Type: LW (100010) & SW (101011) → 00

I-Type: BEQ (000100) → 01

J-Type: J (000010) → XX (Doesn't use the ALU)

<u>OpCodes</u>	<u>ALUOp1</u>	<u>ALUOp0</u>
----------------	---------------	---------------

000000		1	0
--------	--	---	---

100010		0	0
--------	--	---	---

101011		0	0
--------	--	---	---


000100		0	1
--------	--	---	---

000010		x	x
--------	--	---	---

Generating the ALU Control Signals

ALUOp		Func field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111

FIGURE C.2.1 The truth table for the 4 ALU control bits (called Operation) as a function of the ALUOp and function code field. This table is the same as that shown in Figure 5.13.

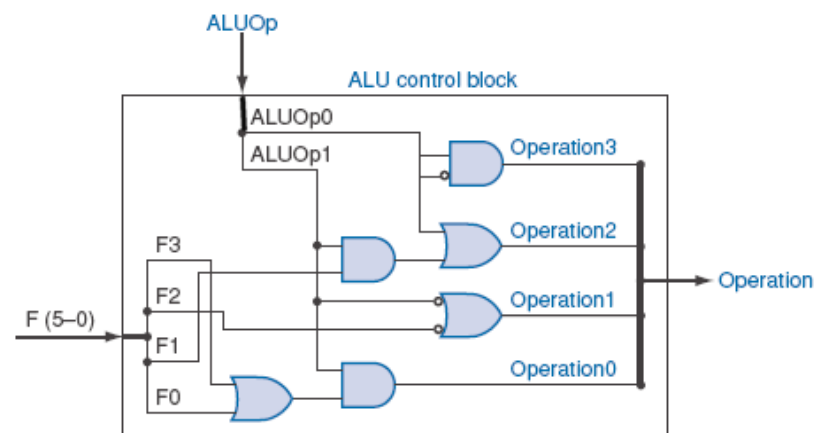

Generating the One Clock Control Signals



Control	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

FIGURE C.2.4 The control function for the simple one-clock implementation is completely specified by this truth table. This table is the same as that shown in Figure 5.22.

Generating the One clock Control Signals

Control	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

FIGURE C.2.4 The control function for the simple one-clock implementation is completely specified by this truth table. This table is the same as that shown in Figure 5.22.

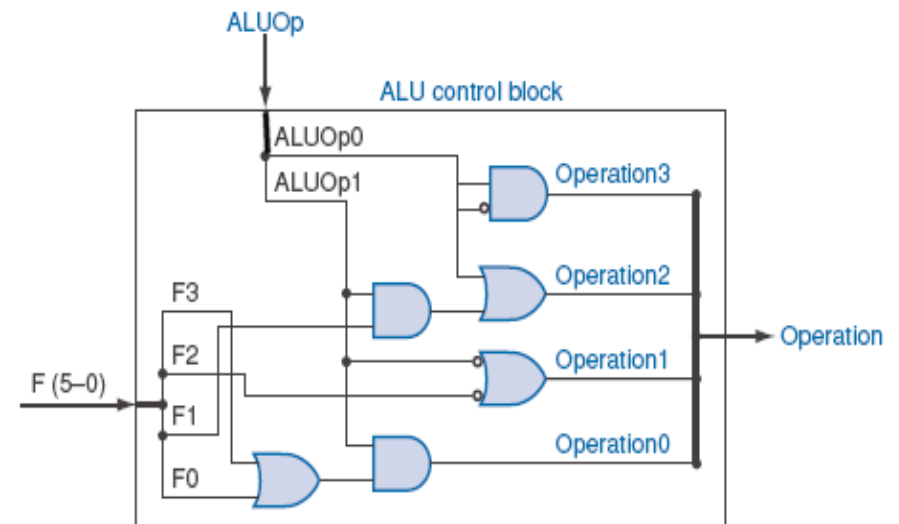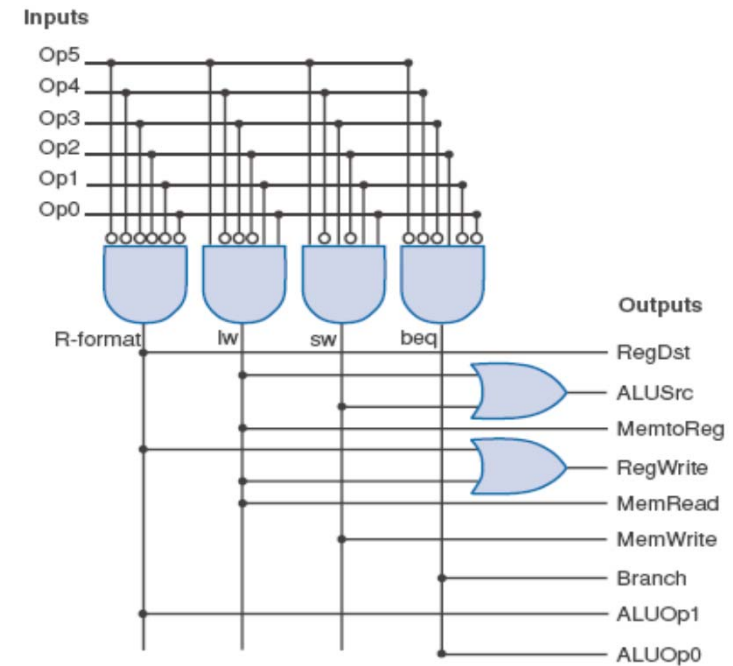

Implementing the Multiple Clock Cycle Machine

- The Multiple Cycle Machine cannot be implemented simply as combinational logic.

Why?

Because each instruction requires 3 -5 states (clock cycles) to complete.

- It will require a Finite State machine (FSM).


A set of states. How many?

Combinational logic for control signals.

Combinational logic for next state inputs.

- It can be implemented with a PLA(s).

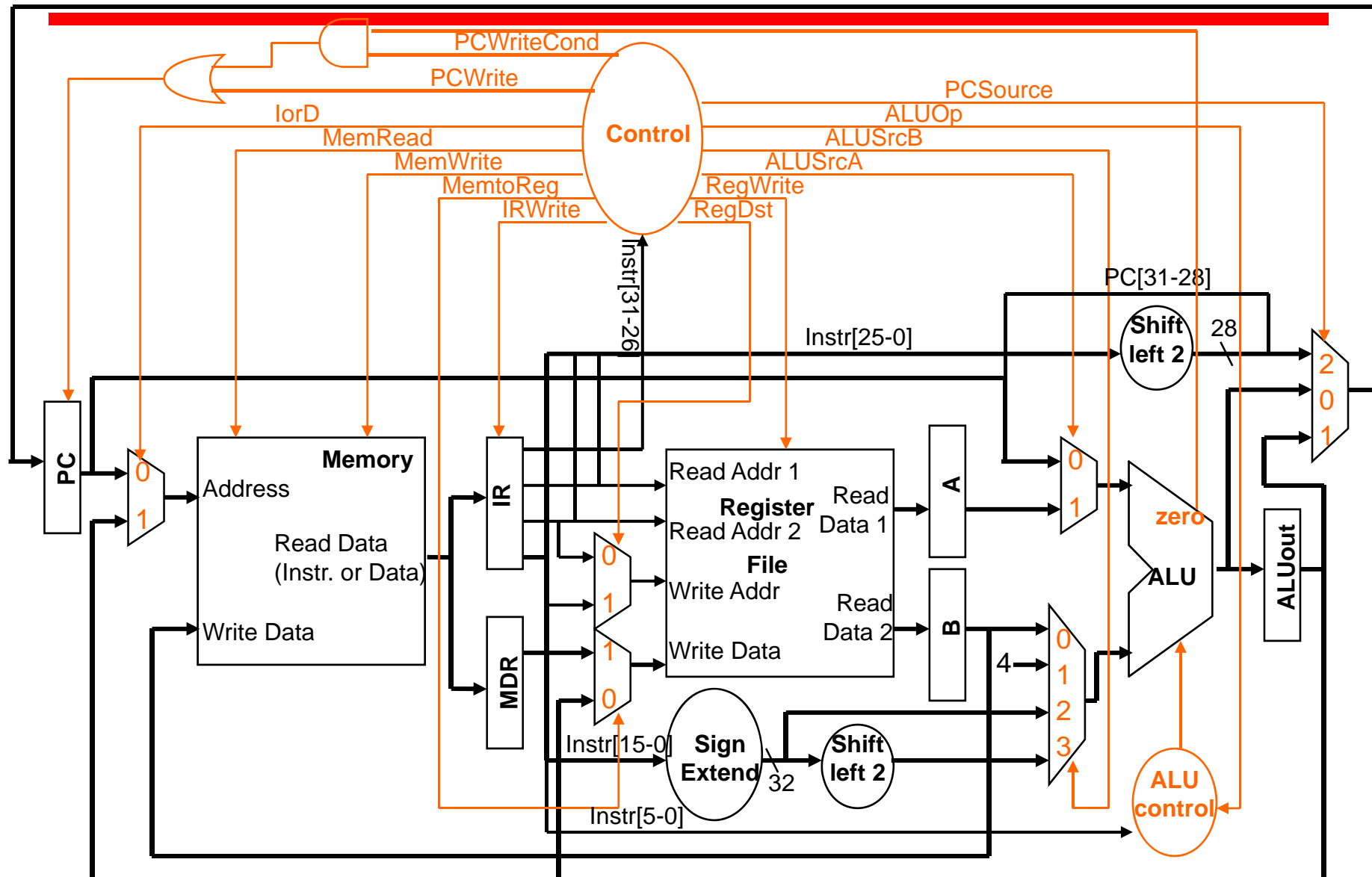The Multicycle Datapath with Control Signals



Multiple Clock Cycle Finite State Machine


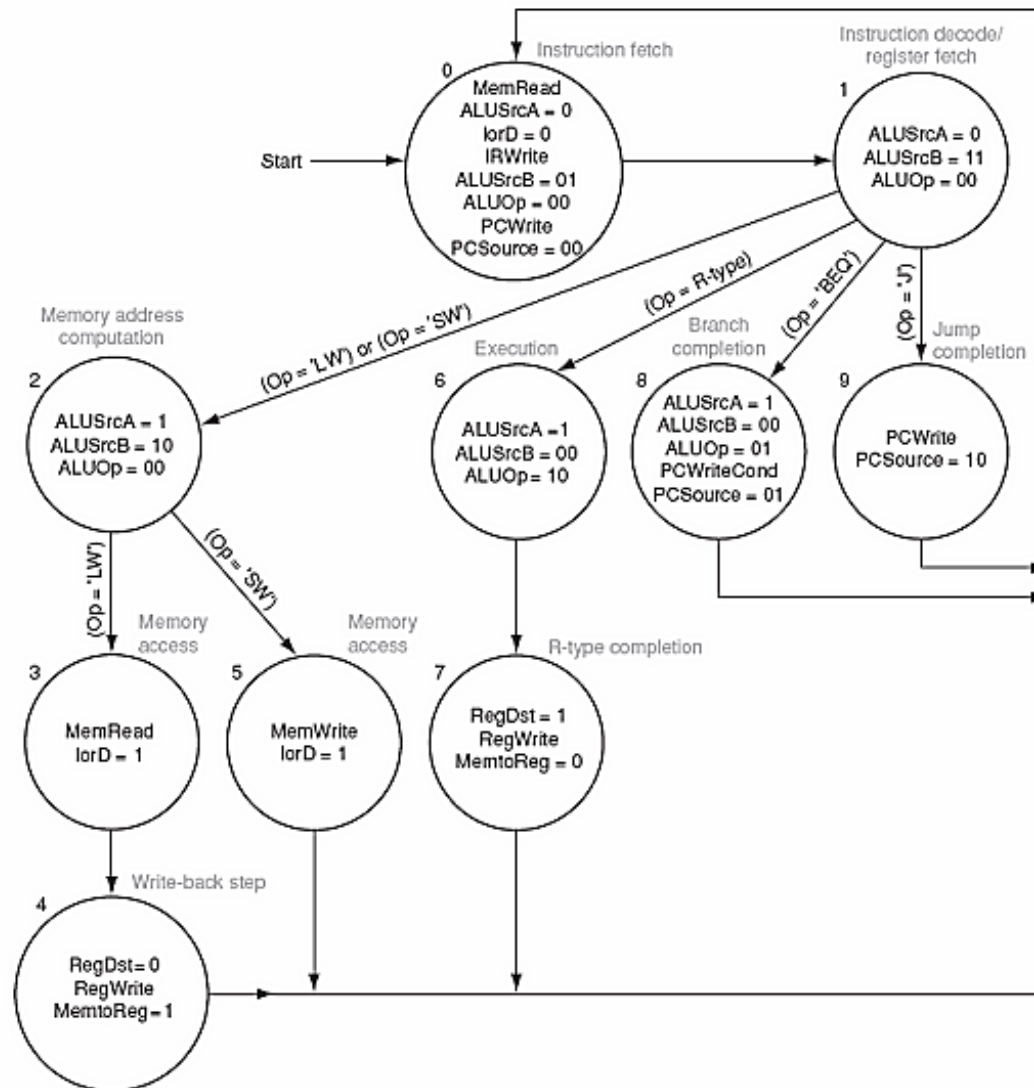
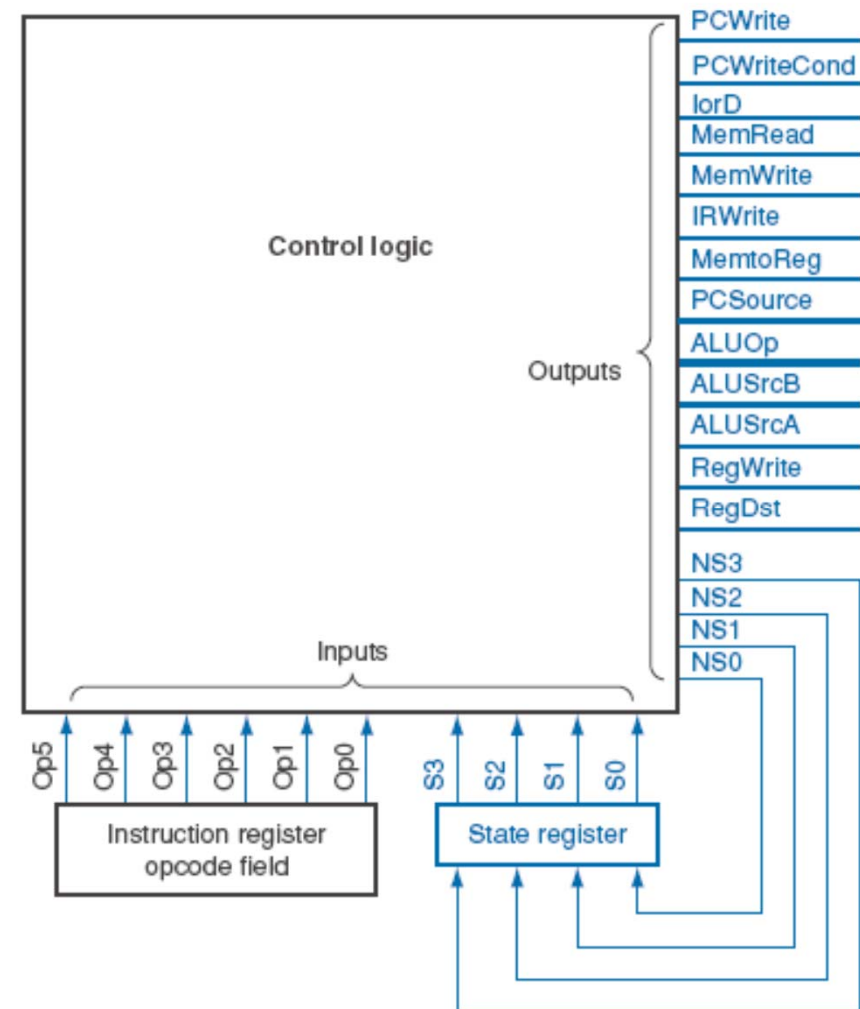


FIGURE C.3.1 The finite-state diagram that was developed in Chapter 5; it is identical to Figure 5.37.

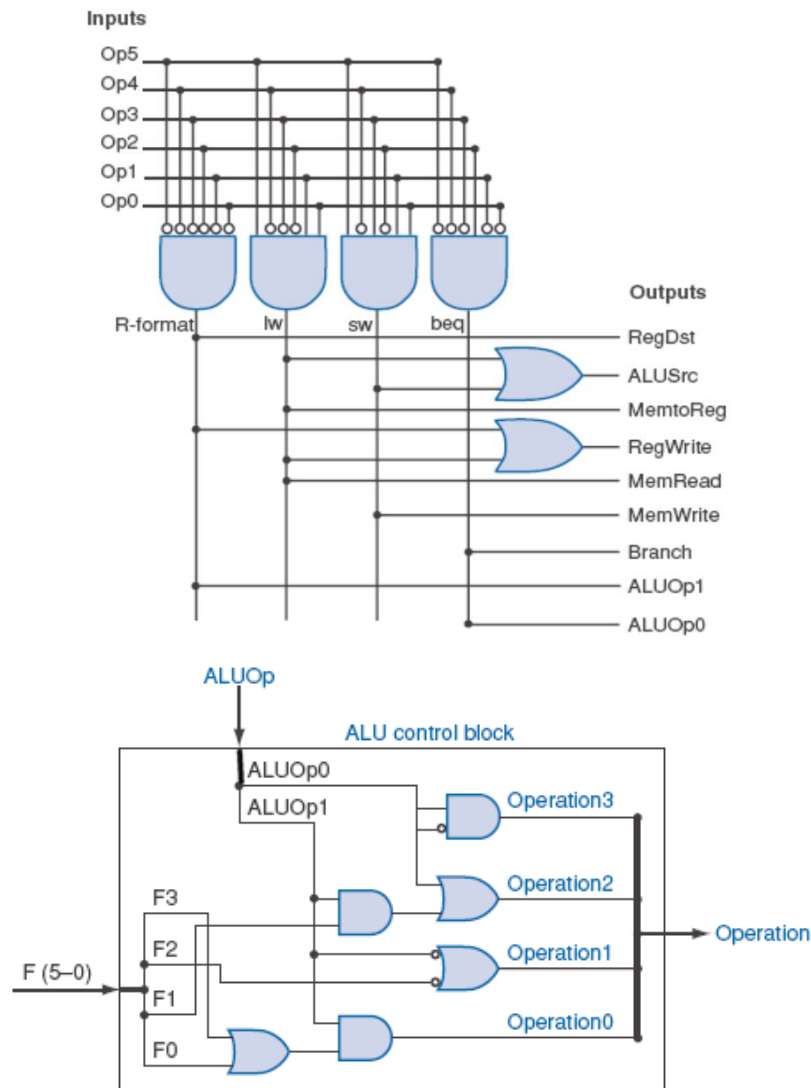Comparing Single and Multiple Clock Machines



Generating the Next State Equations


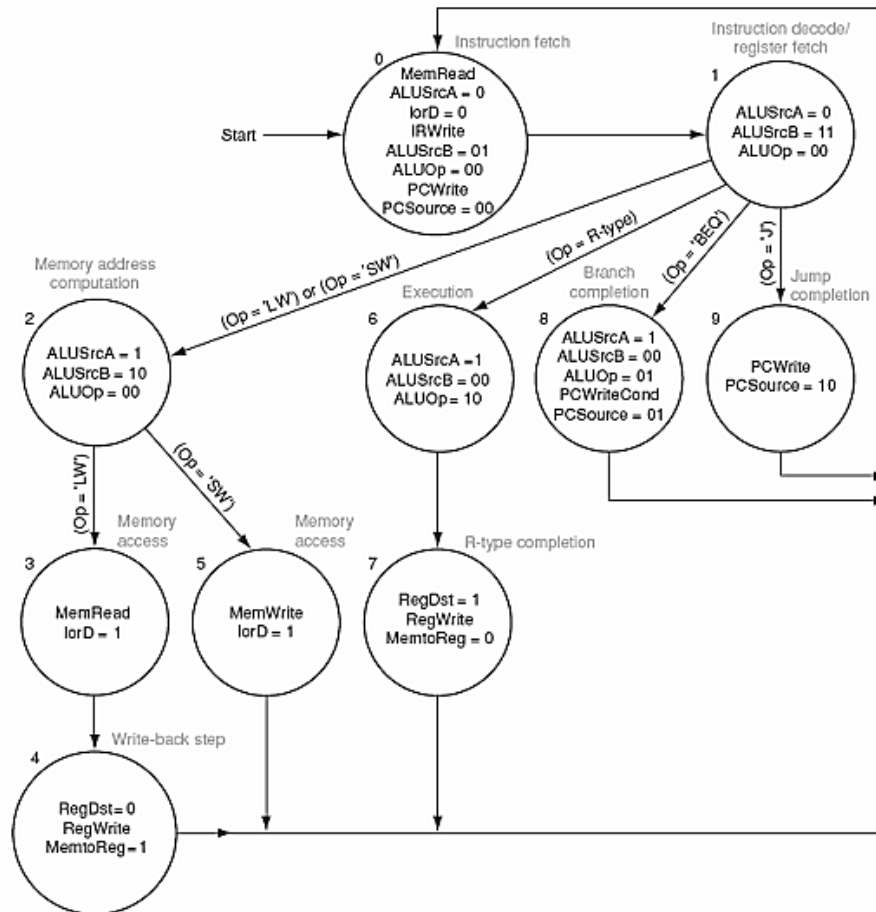
 


FIGURE C.3.1 The finite-state diagram that was developed in Chapter 5; it is identical to Figure 5.37.

Output	Current states	Op
PCWrite	state0 + state9	
PCWriteCond	state8	
lrd	state3 + state5	
MemRead	state0 + state3	
MemWrite	state5	
IRWrite	state0	
MemtoReg	state4	
PCSource1	state9	
PCSource0	state8	
ALUOp1	state6	
ALUOp0	state8	
ALUSrcB1	state1 + state2	
ALUSrcB0	state0 + state1	
ALUSrcA	state2 + state6 + state8	
RegWrite	state4 + state7	
RegDst	state7	
NextState0	state4 + state5 + state7 + state8 + state9	
NextState1	state0	
NextState2	state1	(Op = 'lw') + (Op = 'sw')
NextState3	state2	(Op = 'lw')
NextState4	state3	
NextState5	state2	(Op = 'sw')
NextState6	state1	(Op = 'R-type')
NextState7	state6	
NextState8	state1	(Op = 'beq')
NextState9	state1	(Op = 'jmp')

FIGURE C.3.3 The logic equations for the control unit shown in a shorthand form.

PLA Implementation of Multi Clock FSM

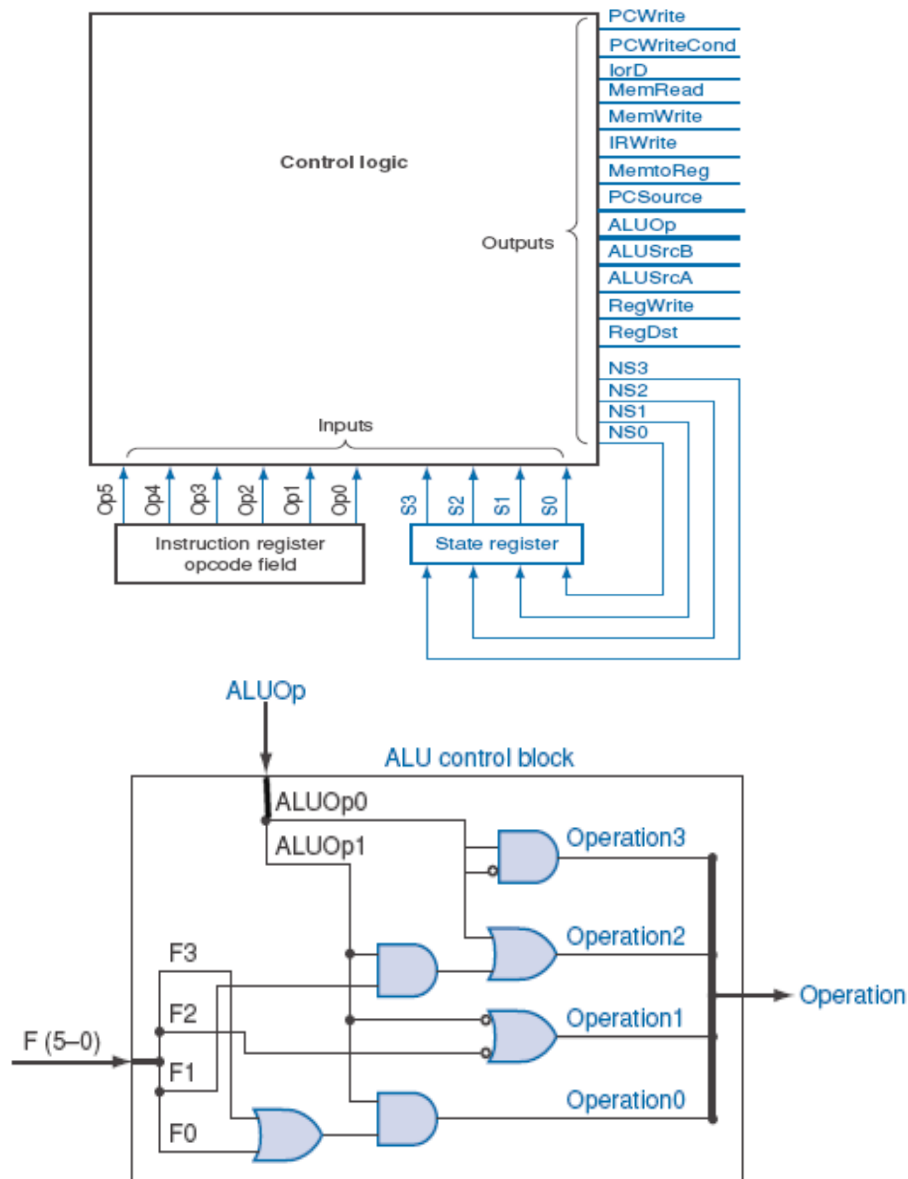

Micro-Programmed Control

- An alternative to a wired implementation.
- Most Computers today are at least partially implemented with Micro-program control
- The concept is to build a simpler internal computer (micro-computer) that implements the control sequences (micro-instructions) that are stored in a micro-computer memory (ROM)
- The advantage is ease of design, flexibility, and adaptability to "families of computers".

Control Unit Organization

The Control Memory contains sequences of microinstructions that provide the control signals to execute instruction cycles, e.g. Fetch, Indirect, Execute, and Interrupt.

Tasks of Control Unit:

- Microinstruction sequencing
- Microinstruction execution

